


CS4341.504 HW#2 - solution

FALL SEMESTER 2023

INSTRUCTOR: DR. ALICE WANG
alice.wang@utdallas.edu

Part 1 - Boolean Theorems (20pts)

Given the following circuit:

 

- Convert the circuit into an equation

$$\neg A \neg B \neg C + \neg A \neg B C + \neg A B \neg C + \neg A B C + A \neg B \neg C + A \neg B C$$

- Convert the circuit/equation into a truth table.

#	A	B	C	f(A, B, C)
0	0	0	0	1
1	0	0	1	1

2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

- Convert the truth table into Sum-of-Products.

$$\text{SOP} = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + \overline{A}B\overline{C} + ABC$$

- Convert the truth table into Product-of-Sums

$$\text{POS} = (A + \overline{B} + C) * (\overline{A} + B + C)$$

- Show the Sigma Notation for the truth table.

$$\Sigma(0,1,3,5,6,7)$$

- Show the Pi Notation for the truth table.

$$\pi(3,5)$$

- Using Boolean Theorems step-by-step simplify the equation to the normalized form. List each theorem used. Underline the sections you will apply the theorem

Use the POS to simplify:


- | | |
|---|-------------------|
| 1. $(A + \overline{B} + C) * (\overline{A} + B + C)$ | T8 Distributivity |
| 2. $A\overline{A} + AB + AC + \overline{A}\overline{B} + \overline{A}B + \overline{A}C + \overline{B}C + \underline{\overline{A}C} + \underline{BC} + \underline{CC}$ | T3 Idempotency |
| 3. $\underline{A\overline{A}} + AB + AC + \overline{A}\overline{B} + \underline{\overline{A}B} + \overline{A}C + \overline{B}C + C$ | T5 Complements |
| 4. $\underline{0} + AB + AC + \overline{A}\overline{B} + \underline{0} + \overline{A}C + \overline{B}C + C$ | T1 Identity |
| 5. $AB + \underline{AC} + \overline{A}\overline{B} + \overline{A}C + \overline{B}C + \underline{BC} + C$ | T6 Commutativity |
| 6. $AB + \overline{A}\overline{B} + \underline{AC} + \overline{A}C + \overline{B}C + \underline{BC} + C$ | T7 Associativity |
| 7. $AB + \overline{A}\overline{B} + (\underline{AC} + \overline{A}C) + (\underline{\overline{B}C} + \underline{BC}) + C$ | T10 Combining |
| 8. $AB + \overline{A}\overline{B} + \underline{C} + \underline{C} + \underline{C}$ | T3 Idempotency |
| 9. $AB + \overline{A}\overline{B} + C$ | final |

- Use Karnaugh-map to simplify the equation to the normalized form
 - o Correctly draw the K-Map and mark the implicants.
 - o List out each of the implicants, and the terms generated.

AB		00	01	11	10
C	0	1	0	1	0
	1	1	1	1	1

$$AB + \neg A \neg B + C$$

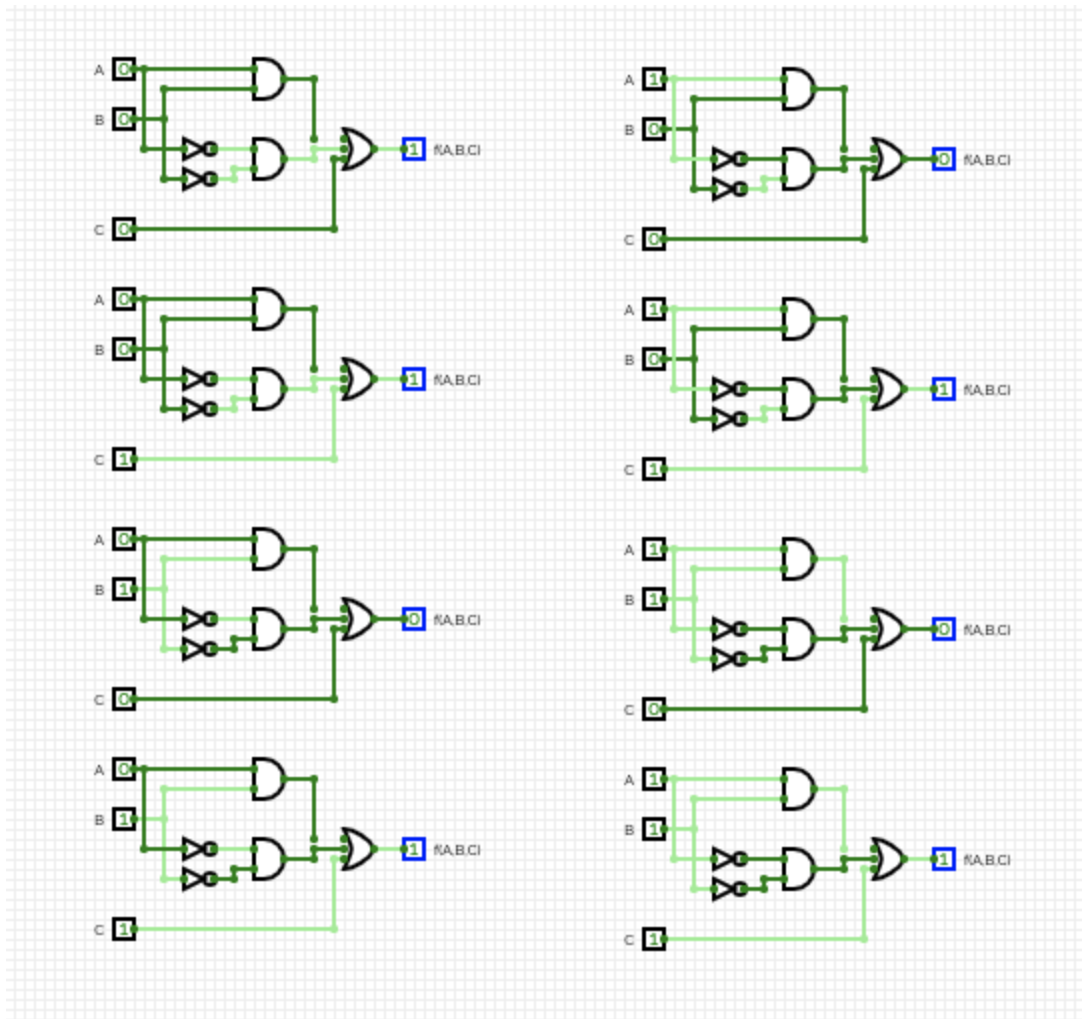
- Draw the schematic of the circuit for the normalized form and verify its function using the circuitverse website. For verification capture screenshots showing the outputs for each input combination (hint: toggle the inputs and verify that the output is correct.)



This matches the Truth Table.

- Write the Verilog code for the circuit and verify its function using edaplayground by showing the waveform of the output with all combinations of inputs.
 
```
# KERNEL: Start
# KERNEL: a:0,b:0,c:0,out:1
# KERNEL: a:0,b:0,c:1,out:1
# KERNEL: a:0,b:1,c:0,out:0
# KERNEL: a:0,b:1,c:1,out:1
# KERNEL: a:1,b:0,c:0,out:0
# KERNEL: a:1,b:0,c:1,out:1
# KERNEL: a:1,b:1,c:0,out:1
# KERNEL: a:1,b:1,c:1,out:1
```



- Submit your work (PDF format). For the schematic from circuitverse and the waveform window from edaplayground use a screen capture utility and cut-n-paste to your report.

Part 2 - Evaluate Boolean Expressions (10pts)

Evaluate the Boolean equation

$$F = a \text{ AND } (b \text{ OR } (c \text{ AND } d))$$

for the given values of variables a, b, c, and d:

1. a=1, b=1, c=0, d=1
2. a=0, b=0, c=0, d=1
3. a=1, b=0, c=0, d=0
4. a=1, b=0, c=1, d=1
5. a=1, b=0, c=0 d=1

- 1) $F = 1 \text{ AND } (1 \text{ OR } (0 \text{ AND } 1)) = 1 \text{ AND } (1 \text{ OR } 0) = 1 \text{ AND } 1 = 1$
- 2) $F = 0 \text{ AND } (0 \text{ OR } (0 \text{ AND } 1)) = 0 \text{ AND } (0 \text{ OR } 0) = 0 \text{ AND } 0 = 0$
- 3) $F = 1 \text{ AND } (0 \text{ OR } (0 \text{ AND } 0)) = 1 \text{ AND } (0 \text{ OR } 0) = 1 \text{ AND } 0 = 0$
- 4) $F = 1 \text{ AND } (0 \text{ OR } (1 \text{ AND } 1)) = 1 \text{ AND } (0 \text{ OR } 1) = 1 \text{ AND } 1 = 1$
- 5) $F = 1 \text{ AND } (0 \text{ OR } (0 \text{ AND } 1)) = 1 \text{ AND } (0 \text{ OR } 0) = 1 \text{ AND } 0 = 0$

Part 3 - Multiplexors & Adders (50pts)

In part we will create combinational logic subcircuits which are building blocks for a small processor in future assignments.

In circuitverse.org, create


- 2:1 mux using two-level logic
- 2:1 mux using tristate buffers
- half-adder

For verification capture screenshots showing the outputs for all input combinations (hint: toggle the inputs and verify that the output match the truth table.)


2:1 mux truth table:

sel	b	a	y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

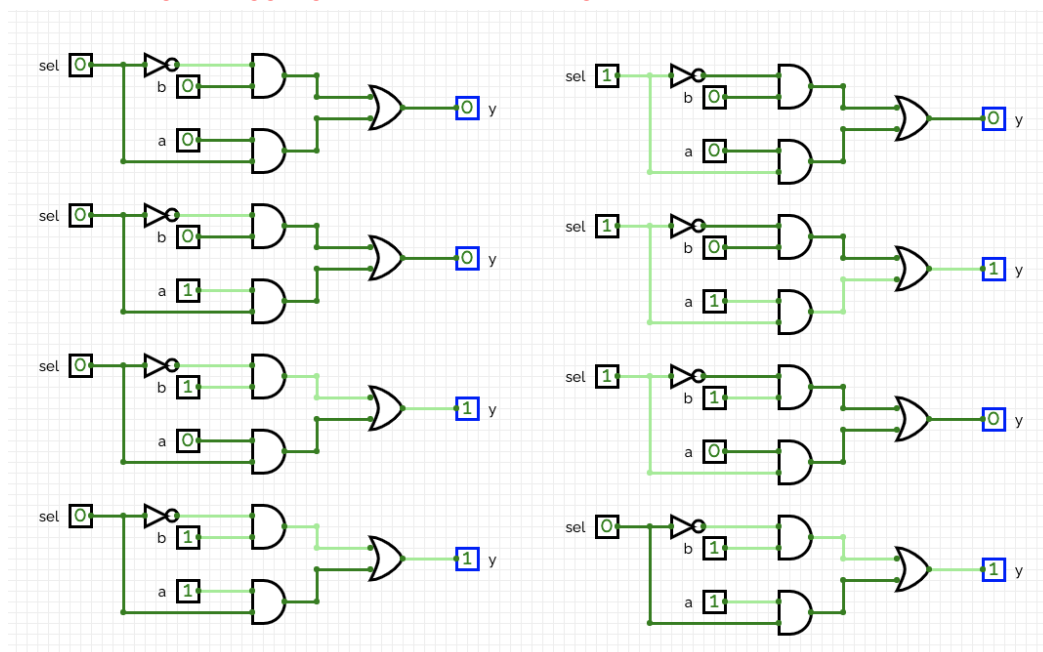Two-level logic - toggling inputs and matching the truth table



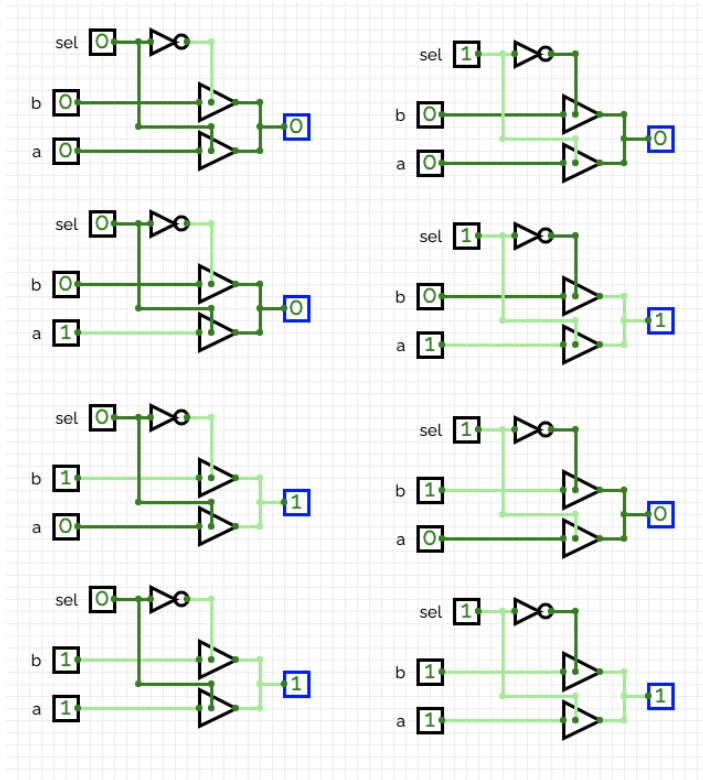
Tristate buffer - toggling inputs and matching the truth table



Half-adder truth table

b	a	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

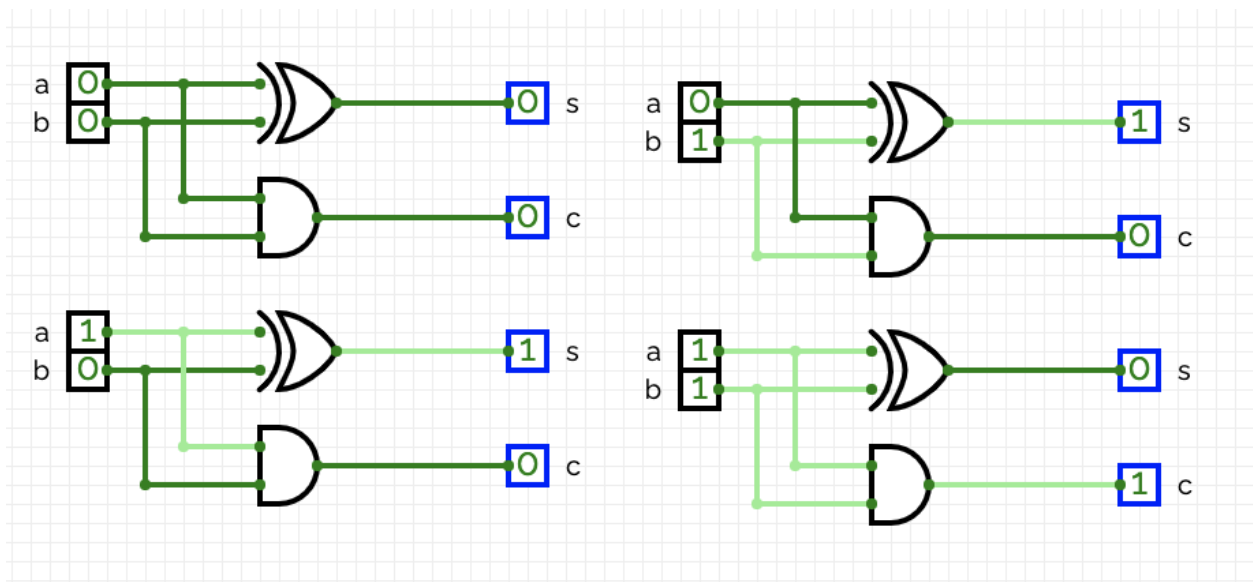Half-adder toggling the inputs and matching the truth table



- Write the Verilog code for a 2:1 mux and half-adder and verify their functionality using edaplayground.com by creating a testbench that tests all input combinations.

Verilog code: testbench instantiation

```

1 // Testbench
2 module test;
3
4     reg a,b,sel,y1, y2, s, c;
5
6     // Instantiate design under test
7     mux2_two_stage_logic MYMUX0 (.a(a), .b(b), .sel(sel), .y(y1));
8     mux2_tristate MYMUX1 (.a(a), .b(b), .sel(sel), .y(y2));
9     half_adder HA (.a(a), .b(b), .s(s), .c(c));
10
11     initial begin
12         // Dump waves
13         $dumpfile("dump.vcd");
14         $dumpvars(1);
15
16         $display("Start");
17         {sel,b,a} = 3'b000;
18         display;
19         {sel,b,a} = 3'b001;
20         display;
21         {sel,b,a} = 3'b010;
22         display;
23         {sel,b,a} = 3'b011;
24         display;
25         {sel,b,a} = 3'b100;
26         display;
27         {sel,b,a} = 3'b101;
28         display;
29         {sel,b,a} = 3'b110;
30         display;
31         {sel,b,a} = 3'b111;
32         display;
33         {sel,b,a} = 3'b000;
34         display2;
35         {sel,b,a} = 3'b001;
36         display2;
37         {sel,b,a} = 3'b010;
38         display2;
39         {sel,b,a} = 3'b011;
40         display2;
41     end
42 
```

Verilog code: design instantiation

// Design

```
module mux2_two_stage_logic (a,b,sel,y);
    input a,b,sel;
    output y;

    assign y = (sel & a) | (~sel & b);
endmodule

module tristate_buffer (a,sel,y);
    input a,sel;
    output y;

    assign y = sel ? a : 1'bZ;
endmodule

module mux2_tristate (a,b,sel,y);
    input a,b,sel;
    output y;

    tristate_buffer TR1 (a,sel,y);
    tristate_buffer TR2 (b,~sel,y);
endmodule

module half_adder (a,b,s,c);
    input a,b;
    output s,c;


    assign s = a ^ b;
    assign c = a & b;
endmodule
```

- Submit your work (PDF). For the schematic from circuitverse and the waveform window from edaplayground use a screen capture utility and cut-n-paste to your report by the due date.


Part 4 - Transistors (20pts)

Show the pull-up/pull-down path for the 3-input NOR that was shown in Lecture 4 when

 - (a) $a=1, b=0, c=1$
- (b) $a=0, b=0, c=0$



(a)

 

(b)